



University of British Columbia
Electrical and Computer Engineering
EECE281/EECE282

Project 2: Electromagnetic Tether Robot.

Dr. Jesús Calviño-Fraga P.Eng.
Department of Electrical and Computer Engineering, UBC
Office: KAIS 3024
E-mail: jesusc@ece.ubc.ca
Phone: (604)-827-5387

March 16, 2015

Project 2 Description

Copyright © 2012-2015, Jesús Calviño-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

1

Requirements


- F38x Microcontroller Board (two required!):
 - Robot is the receiver. It keeps a preprogrammed and configurable distance from the remote (transmitter).
 - Remote is the transmitter. It sends the beacon and commands to the Robot.
- Programmed in C.
- Battery powered.
- Discrete MOSFET drivers.
- Remote commands:
 - Move farther.
 - Move closer.
 - Rotate 180°.
 - Turn Front LED on/off .
 - Turn Back LED on/off .
 - Beep for one second.
 - Parallel park.
- Smallest maximum distance of 100 cm or so. An acceptable range would be 20cm (min.) to 100cm (max.).
- At least one 7-segment to display remote command.

Project 2 Description

Copyright © 2012-2015, Jesús Calviño-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

2

EM Tether Robot

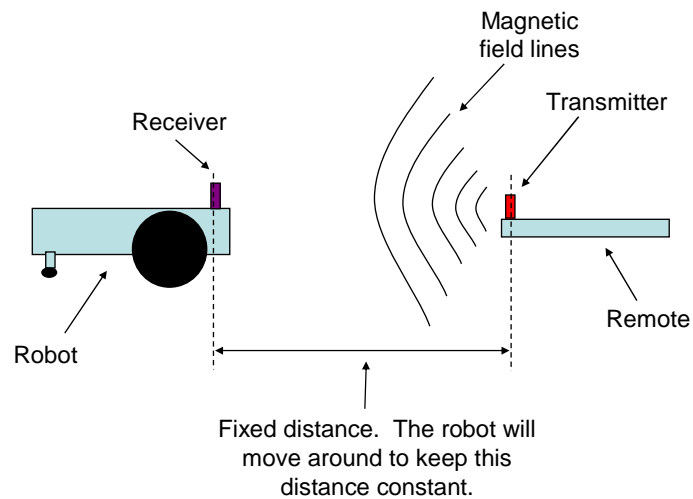


Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

3

EM Tether Robot

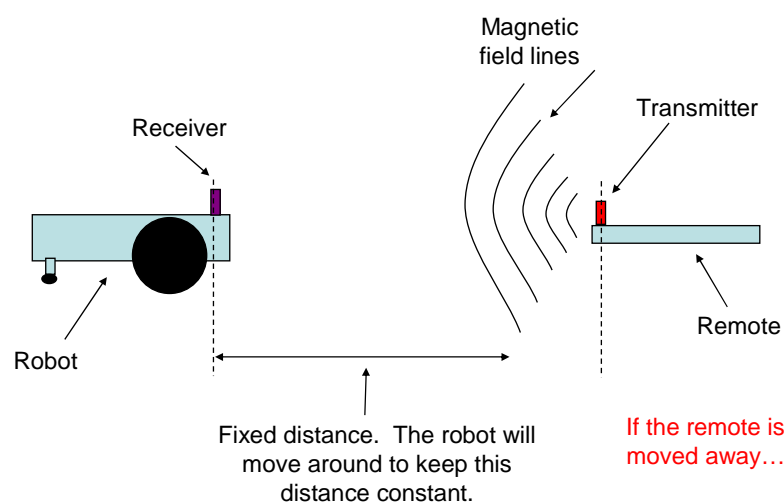


Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

4

EM Tether Robot

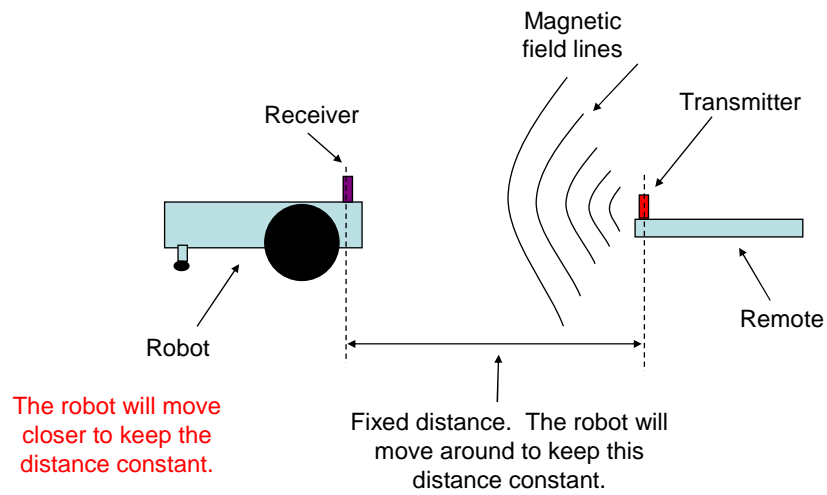


Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

5

EM Tether Robot

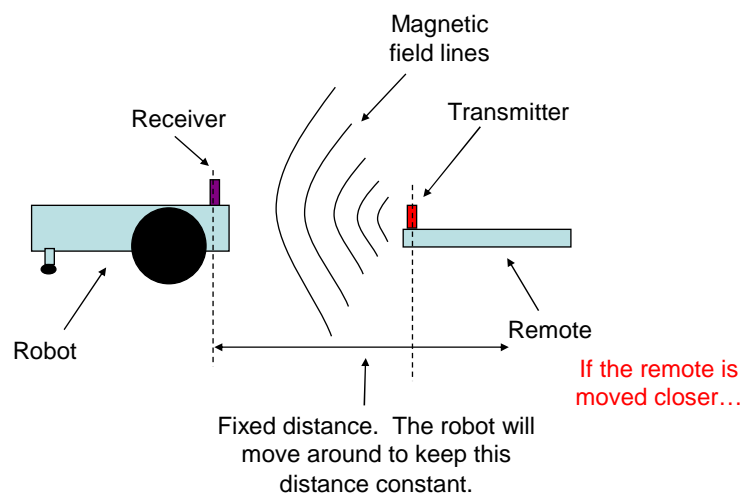


Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

6

EM Tether Robot

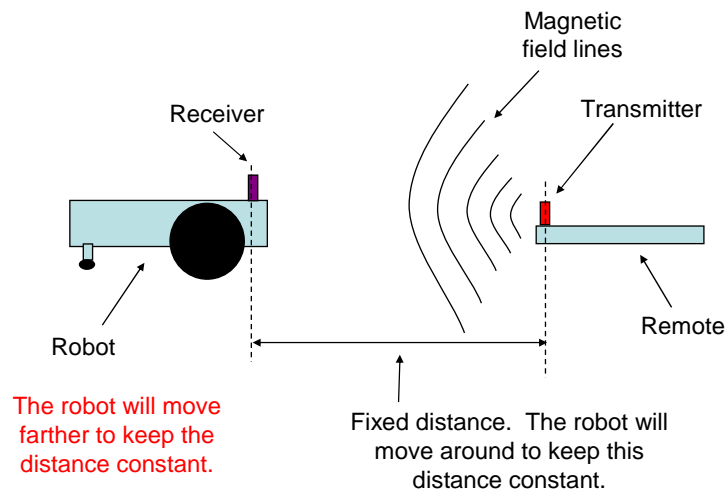

Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

7

Transmitter


- It is a series RLC circuit you should know from EECE253.
- The inductor (L) is provided in the robot kit. You can use any inductor you want!
- For the capacitor (C) you can use the capacitors you already have, but they may not work very well. Optionally you can buy a much better capacitor in local electronics parts stores.
- You'll need a safe, stable, and reliable transmitter for your project.

Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

8

Simplified RLC Transmitter Circuit

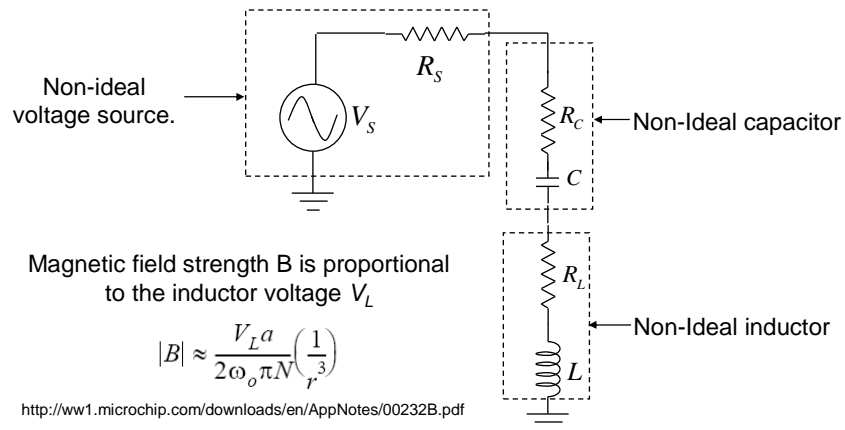


Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

9

Simplified RLC Transmitter Circuit

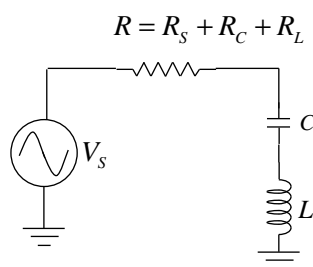

For maximum voltage at the inductor, the circuit must be tuned:

$$f_s = \frac{1}{2\pi\sqrt{LC}}$$


Other factors affect the magnitude of V_L . Use phasor analysis!

Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

10

Simplified RLC Transmitter Circuit

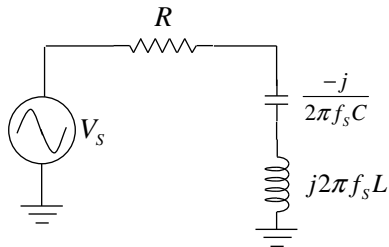

$$i = \frac{V_s}{R - \frac{j}{2\pi f_s C} + j2\pi f_s L} = \frac{V_s}{R}$$

At the tuned frequency this two values are equal!

$$f_s = \frac{1}{2\pi\sqrt{LC}}$$


$$V_L = \frac{jV_s 2\pi f_s L}{R}$$

Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

11

Simplified RLC Transmitter Circuit

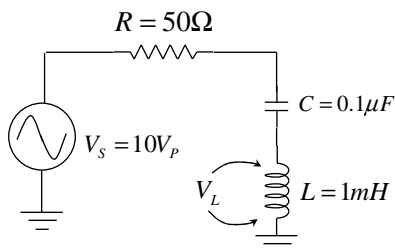

$$f_s = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{1mH \times 0.1\mu F}} = 15.92kHz$$

$$i = \frac{V_s}{R} = \frac{10V_p}{50\Omega} = 0.2A_p$$

$$V_L = j \times 0.2A_p \times 2\pi \times 15.92kHz \times 1mH = 20V_p$$


Not good enough. You'll need 150 to 500 V_p!

Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

12


V_S Using a Function Generator

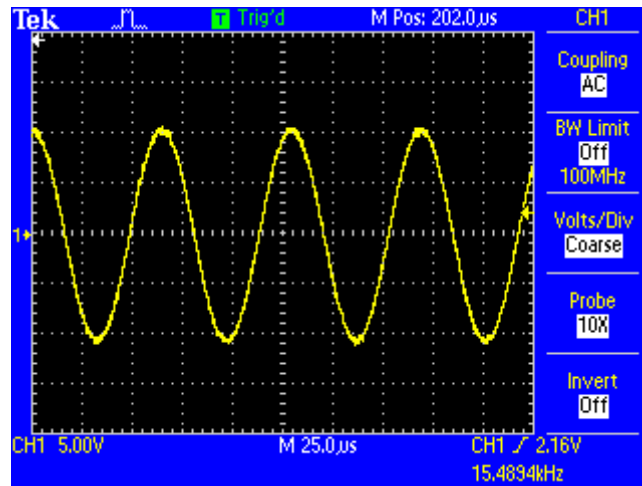

Project 2 Description
Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

13

V_L From the Circuit Above

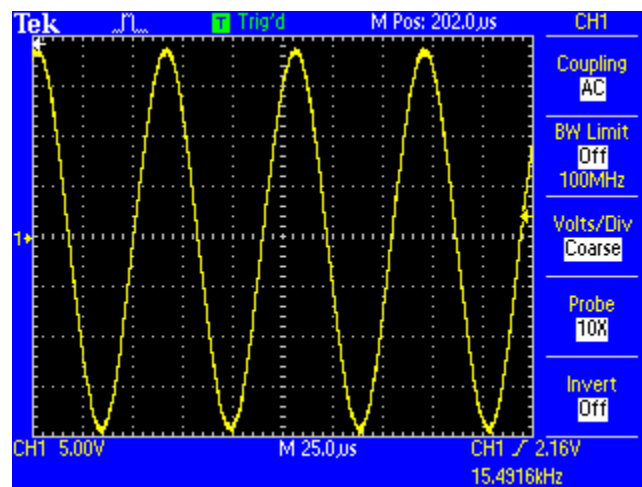

Project 2 Description
Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

14

Maximizing V_L

- Increase V_S .
 - Con: Large source voltages are difficult to handle. Potentially dangerous.
- ~~Increase f_s .~~
 - Con: It won't work because f_s is in the denominator of the magnetic field strength equation. $|B| \approx \frac{V_L a}{2\omega_o \pi N} \left(\frac{1}{r^3}\right)$
- ~~Increase L .~~
 - Con: you'll need to get new inductors. The ones you have are pretty good! Is it also in the magnetic field strength equation?!
- Decrease R .
 - Con: None! Decrease R !

Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

15

V_S

- It can be an square wave!
- The Fourier Series of a square wave is given by:

$$x(t) = \frac{4}{\pi} \sum_{k=1}^{\infty} \frac{\sin(2\pi(2k-1)ft)}{2k-1} = \frac{4}{\pi} \left(\sin(2\pi ft) + \frac{1}{3} \sin(6\pi ft) + \frac{1}{5} \sin(10\pi ft) + \dots \right)$$

↑ Fundamental
 ↑ 3rd harmonic
 ↑ 5th harmonic

Bonus: The amplitude of the fundamental is $4/\pi=1.273$ times the amplitude of the square wave!


Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

16

V_S : you can use an H-bridge!

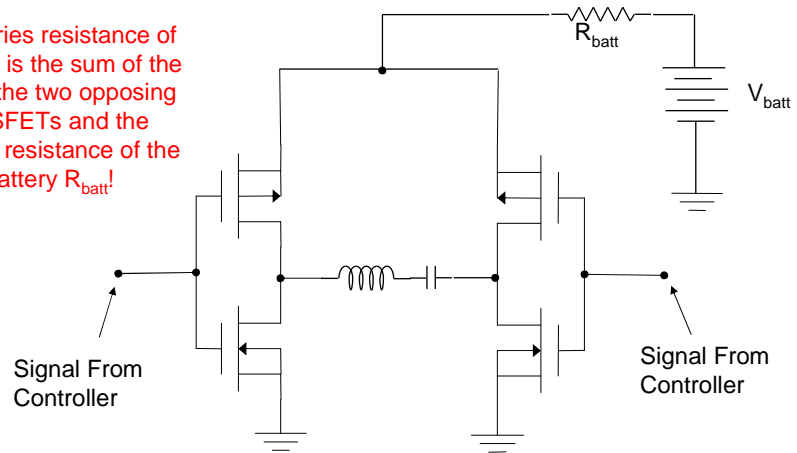The series resistance of this ' V_S ' is the sum of the R_{DS} of the two opposing MOSFETs and the internal resistance of the battery R_{batt} !



Optocouplers may not be fast enough for transmitter frequency!.

Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

17

WARNING!

- If you use a low resistance source, like the H-bridge from the previous slide, the peak voltage at both the inductor and capacitor may increase to hundreds of volts:
 - If you touch the circuit you will get shocked!
 - The capacitor must be rated for the generated voltage. Putting a 50V capacitor into a 300V circuit may result in a blown capacitor and/or weak magnetic field.

Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.


18

The Inductor

- DigiKey part number M8275-ND

Don't drop the inductor.
The core may break!

Type	Wirewound
Material - Core	Ferrite
Inductance	1mH
Tolerance	±20%
Current Rating	1A
DC Resistance	0.55 Ohms

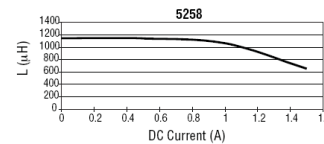

Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

19

The Capacitor

- The peak value of the voltage across the capacitor is equal to the peak value across the inductor. The capacitor **MUST** be rated for the operating voltage! If not:
 - The capacitor may over heat and explode.
 - The capacitor may short circuit and catch fire.
 - The capacitor may introduce too much series resistance.
- Go to RP, Main, or Lee's and buy some good capacitors!


Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

20

The Receiver

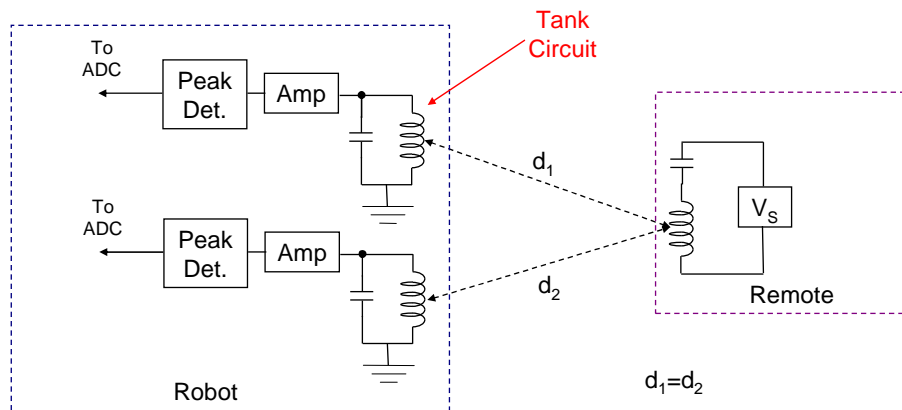- It requires two inductors to determine which way to move:



Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

21

Robot Logic

- If ($d_1 > d$) move motor 1 back.
- If ($d_2 > d$) move motor 2 back.
- If ($d_1 < d$) move motor 1 forward.
- If ($d_2 < d$) move motor 2 forward.
- d is preset after reset, but it can be changed by receiving a command from the remote.

Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

22

Robot Construction

Part #	Description
Solarbotics GM4	Gear Motor 4 - Clear Servo
Lynxmotion Servo Wheel	2.63" x 0.35" (pair) wheels
Tamiya 70144	Ball Caster
4 x AA	Battery holder
1 x 9V cable	9V battery clip
Unfolded chassis	Aluminum chassis made using the water jet cutter.

Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

23

Workshop Safety Training

- You'll need to fold the robot chasis.
- Before using the workshop you'll need to pass the training.
- Training is in MCLD 148.
- Need to register:
 - <http://ece.ubc.ca/tech-services/shop-safety>

Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

24

Fitting the Wheels to the Motors

Question:

“We're finally assembling our rover and the wheels seem to not have the same spline pattern as the motor shaft. I'd rather not force these to mate. Is this unusual? Can you suggest a solution?”

Answer:

The wheels pressure fit into the motor shafts. The wheels are flexible so they will expand a bit making an excellent and tight fit to the shaft. It is hard to press the wheels into the shafts, but if you used the provided screws, you can fit them very easily by screwing them in.

Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

25

Sending Commands From the Remote to the Robot

- Check application note from Microchip. It describes On-Off Keying for data transmission:
<http://ww1.microchip.com/downloads/en/AppNotes/00232B.pdf>
- A minimum of seven commands required:
 - **Move closer.** When the user presses a button in the transmitter, it commands the robot to move closer.
 - **Move farther.** When the user presses a button in the transmitter, it commands the robot to move farther.
 - **Rotate 180°.** When the user presses a button in the transmitter, it commands the robot to rotate 180°.
 - **Parallel park.** When the user presses a button in the transmitter, it commands the robot to parallel park in a space that is 1.5 times the length of the robot.
 - **Turn Front LED on/off.** When the user presses a button (or combination of buttons) in the transmitter, it commands the robot to turn an LED placed at the front of the robot on/off
 - **Turn Back LED on/off.** When the user presses a button (or combination of buttons) in the transmitter, it commands the robot to turn an LED placed at the back of the robot on/off.
 - **Beep for one second.** When the user presses a button (or combination of buttons) in the transmitter, it commands the robot to activate a piezo buzzer (or similar) for one second.


Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

26

Data Bit Rise and Fall Times

FIGURE 5: DATA BIT RISE AND FALL TIMES

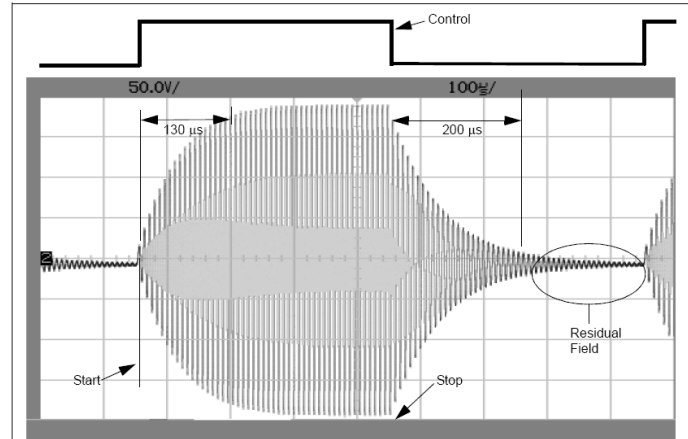


Project 2 Description
Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

27

Data Modulation Formats

FIGURE 6: DATA MODULATION FORMATS

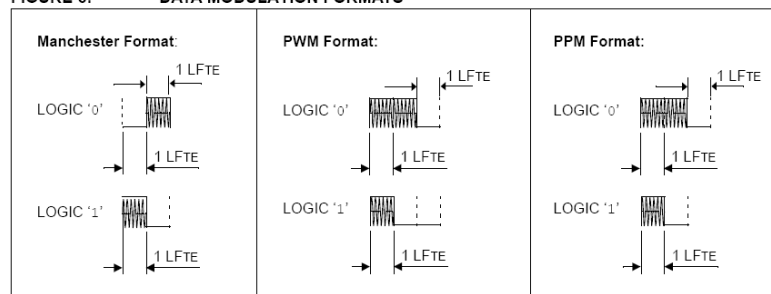

Since you'll need to transmit only a few data bits, it is not a problem to assume 'field present' equal 'logic one' and 'field not present' equal 'logic zero'. The baud rate has to be very low. You can bit bang the transmission and reception as shown in the next slide.

Project 2 Description
Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

28

Bit-bang Transmission/Reception

The 'wait_bit_time()' function must be exactly the same!

```
void tx_byte ( unsigned char val )
{
    unsigned char j;

    //Send the start bit
    txon=0;
    wait_bit_time();
    for (j=0; j<8; j++)
    {
        txon=val&(0x01<<j)?1:0;
        wait_bit_time();
    }
    txon=1;
    //Send the stop bits
    wait_bit_time();
    wait_bit_time();
}
```

Bit-bang transmission in the remote

```
unsigned char rx_byte ( int min )
{
    unsigned char j, val;
    int v;

    //Skip the start bit
    val=0;
    wait_one_and_half_bit_time();
    for(j=0; j<8; j++)
    {
        v=GetADC(0);
        val|=(v>min)?(0x01<<j):0x00;
        wait_bit_time();
    }
    //Wait for stop bits
    wait_one_and_half_bit_time();
    return val;
}
```

Bit-bang reception in the robot

Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

29

Use C8051F38C second UART!

- The C8051F38C comes with two UARTs:
 - UART0: is the standard serial port that comes with most 8051 compatible microcontrollers.
 - UART1: is an enhanced UART available in many Silabs microcontrollers.
- Instead of bit-banging you can just use UART1 with a very slow baud rate.

Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

30

C programmed.

- Both the robot and the remote must be programmed using the C programming language.
- You may 'inline' small portions of assembly code, but the bulk of your code must be C.

Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

31

Battery powered.

- Your project must be battery powered. This includes the electronics and motors of both the transmitter and receiver
- A 9 volt battery strap and a 4 x AA battery holder are included in the parts kit for this project.
- You can use any kind of batteries you want, provided that you acquire the batteries and the holders yourself.
- **WARNING:** batteries are neither included in the parts kits nor they will be provided in the lab. You must buy your own batteries.

Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

32

New Project 2 Due Dates

Function demo: April 7 and 8

Report: April 10

Project 2 Description

Copyright © 2012-2015, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.

33